


PHY 117 HS2023

Week 9, Lecture 2

Nov. 15th, 2023

Prof. Ben Kilminster
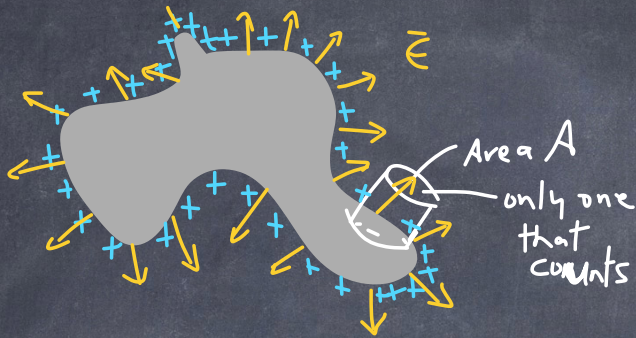
$$E = \frac{\sigma}{\epsilon_0} \text{ close to a conductor}$$



Near surface, $\vec{E} \parallel \hat{n}$
Also, for a conductor, charge is on surface,


$$\oint_S \vec{E} \cdot \hat{n} dA = \frac{Q}{\epsilon_0}$$

$$\sigma = \frac{Q}{A} \quad Q = \sigma A$$

$$E A = \frac{\sigma A}{\epsilon_0}$$

$$\vec{E} = \frac{\sigma}{\epsilon_0} \hat{n} \text{ normal to surface}$$


Capacitors :

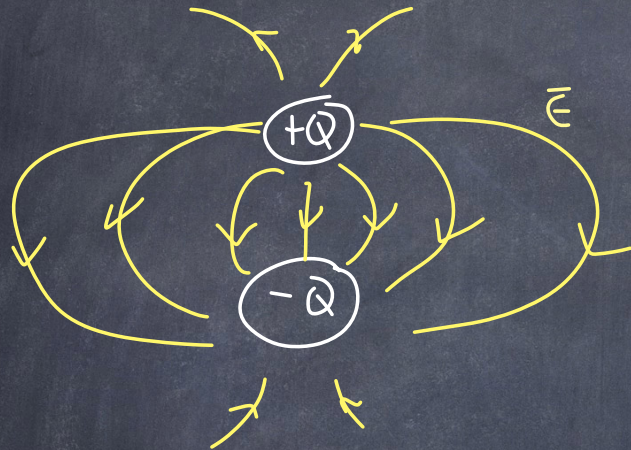

Any two oppositely charged conductors form a capacitor

In a circuit diagram, the symbol for a capacitor is $\text{---}||\text{---}$ or $\text{---}|\text{E}|\text{---}$

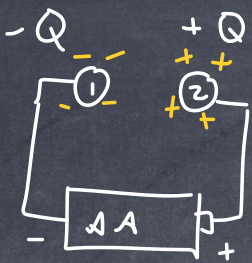we can charge a capacitor by connecting each conductor to the opposite terminals of a battery.



$$\Delta V = 1.5 \text{ V}$$

Q on 1 is opposite to Q on 2.
There is a potential difference between the conductors, ΔV

We define the capacitance as $\frac{Q}{|\Delta V|} \equiv C$


The capacitance is the ability of 2 conductors to store electrical energy.

The units of capacitance are
1 Farad = 1 F = $1 \frac{\text{C}}{\text{V}}$

Energy stored in a capacitor:

$$U = \frac{1}{2} C (\Delta V)^2$$

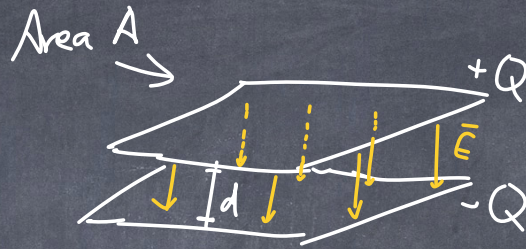what is the capacitance of a parallel-plate capacitor, with area A , separation d , and a charge $+Q$, $-Q$



we know that $E = \frac{\sigma}{\epsilon_0}$, $\sigma = \frac{Q}{A} \Rightarrow E = \frac{Q}{\epsilon_0 A}$ ①


The field is uniform between the 2 plates.

$$|\Delta V| = \left| -\int_0^d \vec{E} \cdot d\vec{l} \right| = E d \stackrel{\text{①}}{=} \frac{Q d}{\epsilon_0 A}$$

$$C = \frac{Q}{|\Delta V|} = \frac{\cancel{Q}}{\frac{\cancel{Q} d}{\epsilon_0 A}} = \frac{\epsilon_0 A}{d}$$

$$C = \frac{\epsilon_0 A}{d}$$

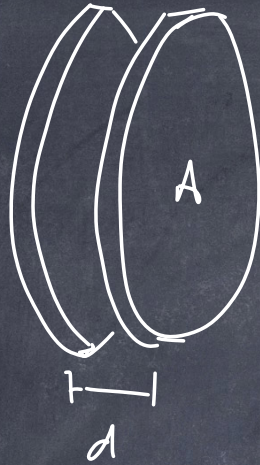capacitance only depends on the dimensions,



← capacitance is $C = \frac{\epsilon_0 A}{d} = \frac{Q}{|\Delta V|}$

$$|\Delta V| = \frac{Qd}{\epsilon_0 A}$$

If we put Q on our capacitor,
and increase d , then ΔV increase


Energy stored in a capacitor

$$U = \frac{1}{2} C (\Delta V)^2$$

$$U = \frac{1}{2} \frac{\epsilon_0 A}{d} E^2 d^2$$

$$= \frac{1}{2} \epsilon_0 A E^2 d$$

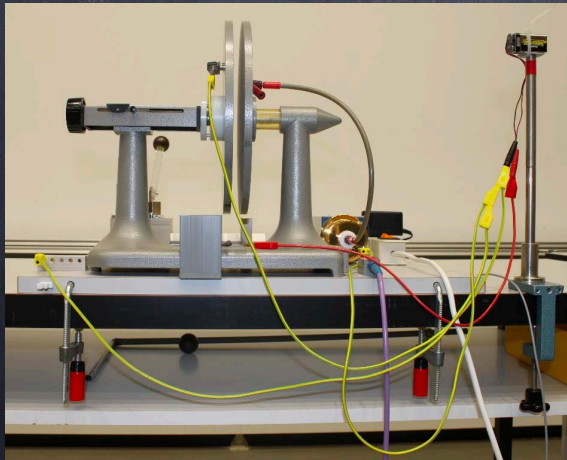So we do work to increase
the stored energy.



Dielectrics - In a non-conducting material, we know that dipoles tend to align opposite to the \vec{E} -field

\vec{E} -field of the dipole itself



The \vec{E} -fields of the dipoles sum up

$$\text{total } \vec{E} \text{ inside} = \vec{E}_{\text{external}} - \vec{E}_{\text{dipoles}}$$




we call the non-conducting material a dielectric.
Each material has its own dielectric constant, K_d
that weakens the electric field,

such that $E = \frac{E_0}{K_d}$ E_0 : E-field with no dielectric
 E : E-field with dielectric

materials	K_d Dielectric constant (no units)
air	1.00059
water	80
paper	3.7
parafin	2
plexiglass	3.4

note: $K_d > 1$

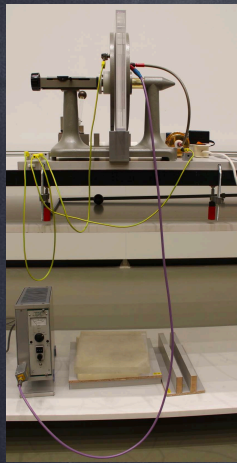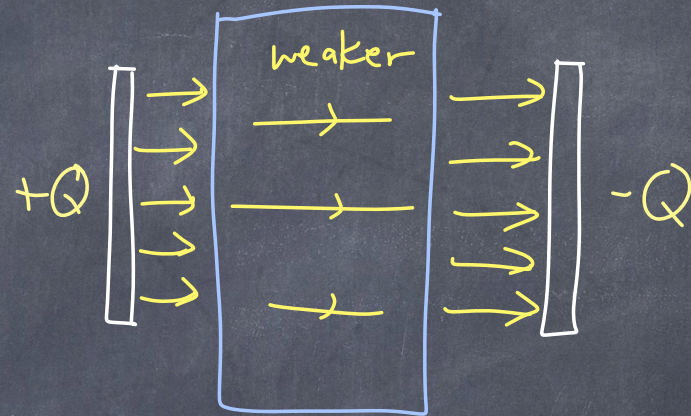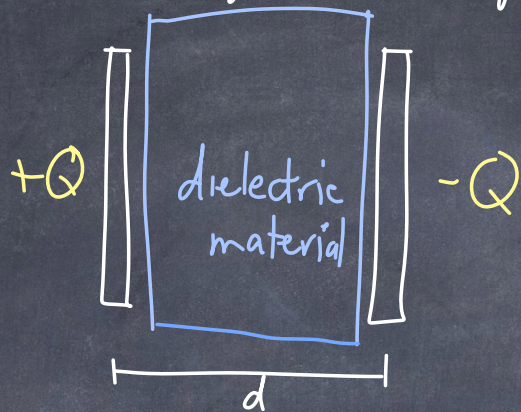Parallel-plate capacitor with a dielectric



Initially, we have $\Delta V_0 = E_0 d$ with no dielectric
 $|\Delta V_0| = E_0 d$

And we know that $\epsilon = \frac{\epsilon_0}{k_d}$, so


we can get $\Delta V = E d = \frac{\epsilon_0 d}{k_d} = \frac{|\Delta V_0|}{k_d} \Rightarrow$ Adding dielectric decrease ΔV

$$\text{So } C = \frac{Q}{|\Delta V|} = \frac{Q k_d}{V_0} = k_d C_0$$

$$\text{For our parallel plate capacitor: } C = k_d \frac{\epsilon_0 A}{d}$$

Combining capacitors:

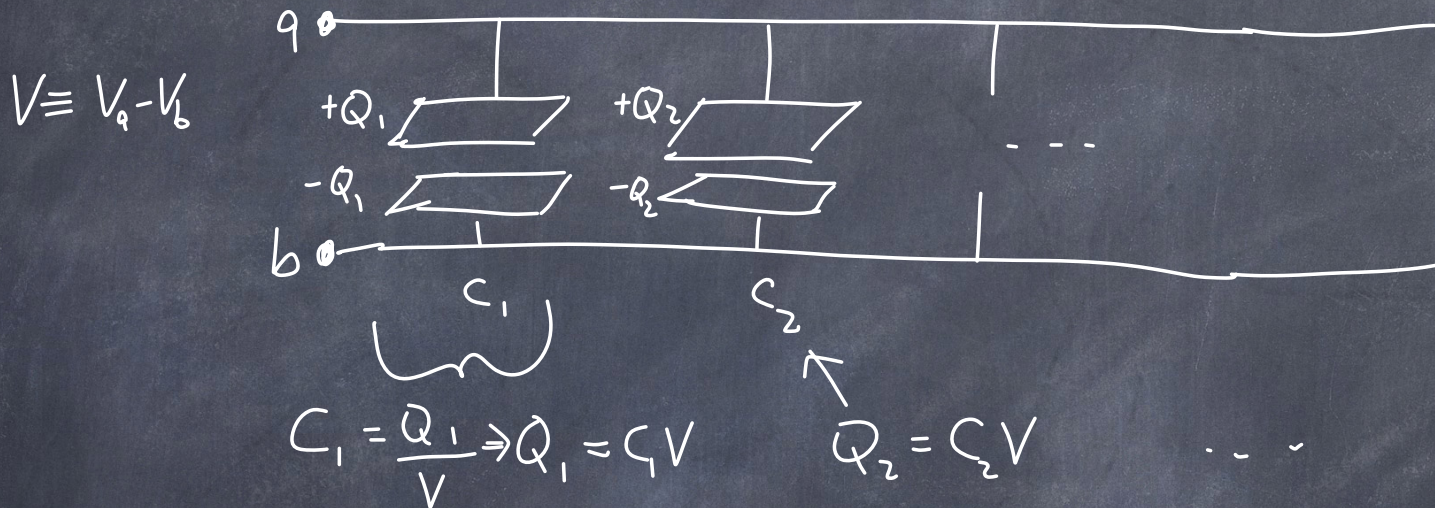when we combine capacitors in parallel,
the capacitors are at the same potential



$$C_1 = \frac{Q_1}{V} \Rightarrow Q_1 = C_1 V \quad Q_2 = C_2 V \quad \dots$$

The total charge stored is $Q = Q_1 + Q_2 = C_1 V + C_2 V$


$$\text{so } Q = (C_1 + C_2) V$$

The equivalent capacitance of parallel capacitors

is


$$C_{eq} = C_1 + C_2 + \dots = \frac{Q}{V}$$

Combining capacitors in series:

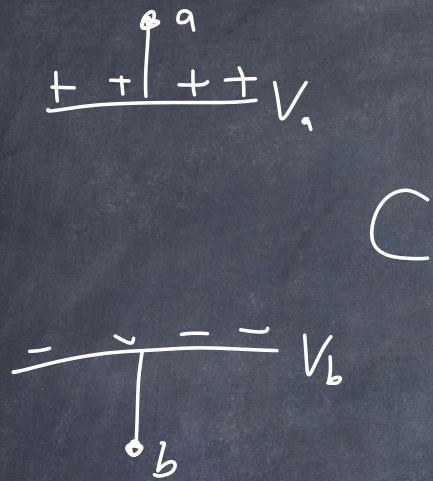

$$V = V_a - V_b$$

$$V = \frac{Q}{C}$$

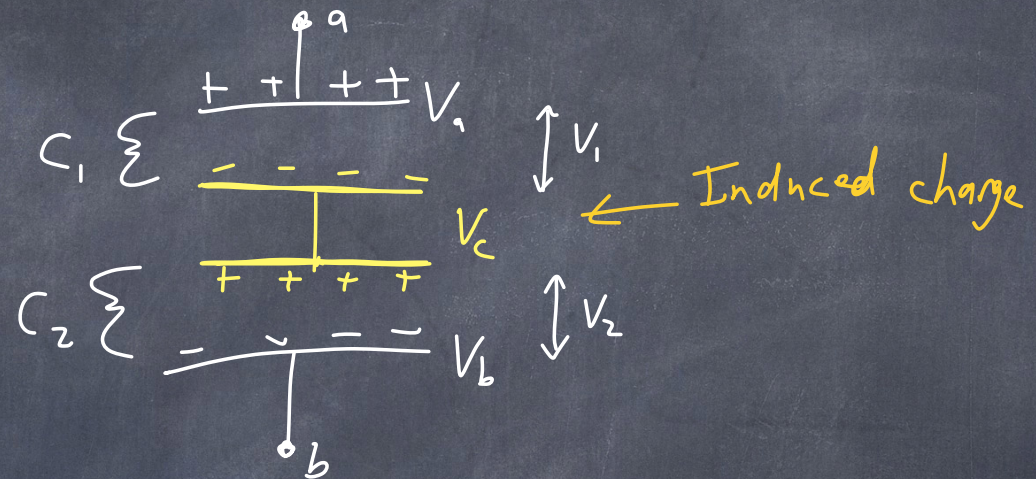

$$V_1 = V_a - V_c \quad V_2 = V_c - V_b$$

$$V_1 = \frac{Q}{C_1} \quad V_2 = \frac{Q}{C_2}$$

The total potential difference $V = V_a - V_b$

$$\text{so } V = V_a - V_b = (V_a - V_c) + (V_c - V_b) = \frac{Q}{C_1} + \frac{Q}{C_2}$$

$$V = Q \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots \right)$$

In general,

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$$

rule for adding capacitors
in series.

$$\text{If } C_1 = 2\mu\text{F} \quad C_2 = 2\mu\text{F}$$

stronger \rightarrow In parallel: $C_{eq} = C_1 + C_2 = 4\mu\text{F}$

weaker \rightarrow In series: $\frac{1}{C_{eq}} = \frac{1}{2\mu\text{F}} + \frac{1}{2\mu\text{F}} \Rightarrow C_{eq} = 1\mu\text{F}$

Since $U = \frac{1}{2} C \Delta V^2 \Rightarrow$ energy is more when
capacitors are in parallel



Capacitors in parallel
vs.
in series

↑
more energy,
more spark.

Electrostatics: $E=0$ in a conductor, V is the same everywhere in a conductor.

Electrodynamics: Current: rate of flow of electric charge.

current $\rightarrow I = \frac{\Delta Q}{\Delta t}$


ΔQ \leftarrow charge
 Δt \leftarrow time

units $[\frac{C}{s}] = 1A$

Amp = Ampere = A


consider a conductor

$\vec{E} = 0$

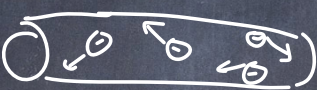


Free electrons in conductor move randomly due to thermal movement
 $v \sim 10^6$ m/s

$\vec{E} \neq 0$

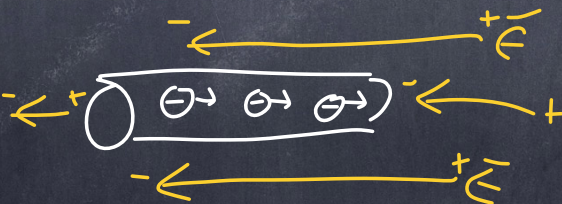


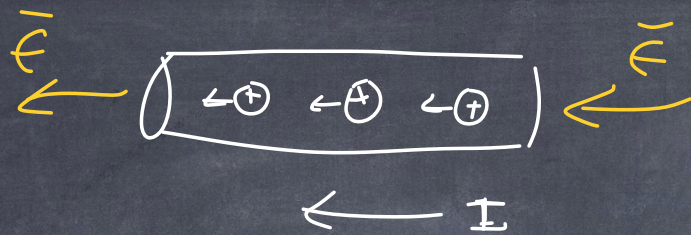Electrons move in direction opposite to the E -field



By convention, the current I moves in the direction that positive charges would move.
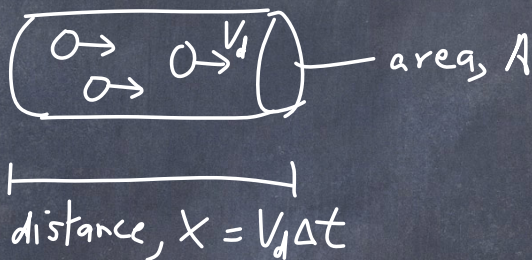
$$n = \frac{\# \text{ charge carriers}}{\text{volume}}$$



V_d : drift velocity
 volume = $A \cdot x = AV_d \Delta t$

Total charge in this cylinder is:

$$\begin{aligned} \Delta Q &= \frac{\# \text{ charge carriers}}{\text{volume}} \cdot \text{volume} \cdot \text{charge per carrier} \\ &= n \cdot \text{volume} \cdot e \end{aligned}$$


$$\Delta Q = n AV_d \Delta t e$$

$$\text{so } I = \frac{\Delta Q}{\Delta t} = \frac{n AV_d \cancel{\Delta t} e}{\cancel{\Delta t}}$$

$$V_d = \frac{I}{n A e} \sim 10^{-5} \frac{\text{m}}{\text{s}} \quad (\text{exercise})$$

If v_d is so slow, why does electricity seem so fast?


Analogy to a hose with water in it.

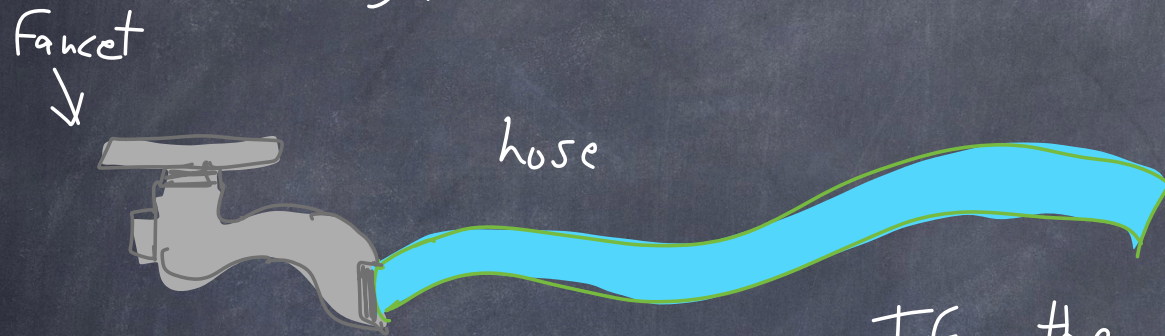

If the hose is already filled with water, then when you turn it on, so the fluid is incompressible, so the flow is instantaneous.

Electricity is \sim instantaneous despite the slow electrons.

Conductor in
an E -field

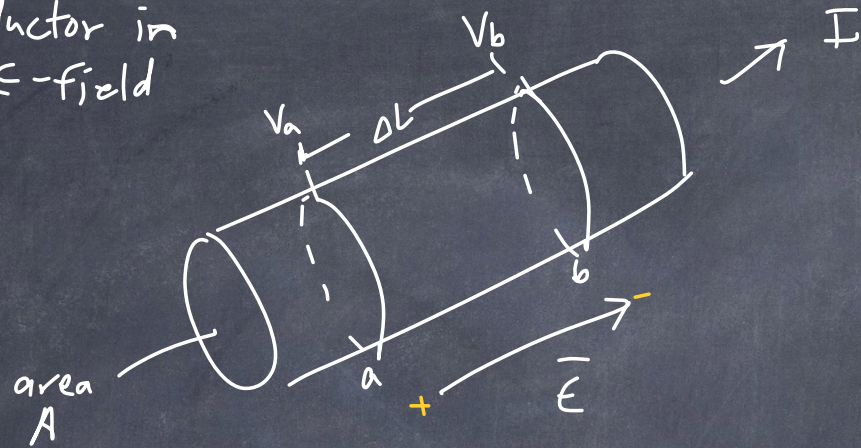

we know that

$$V = V_a - V_b = E \Delta L$$


$$V_a - V_b > 0$$

For most materials, the current is
proportional to the potential difference:

$$I \propto V$$

This constant of proportionality is $\frac{1}{R}$
where R is the resistance of the material

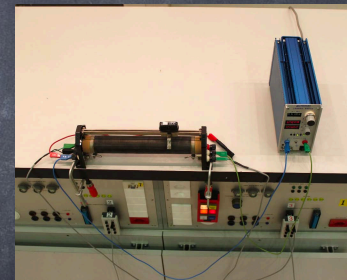
$$I = \left(\frac{1}{R}\right)V \Rightarrow V = IR$$




R has units of Ω (ohms)

where $1 \Omega = 1 \frac{V}{A} = \frac{1 \text{ volt}}{\text{Amp}}$

$$V = IR$$

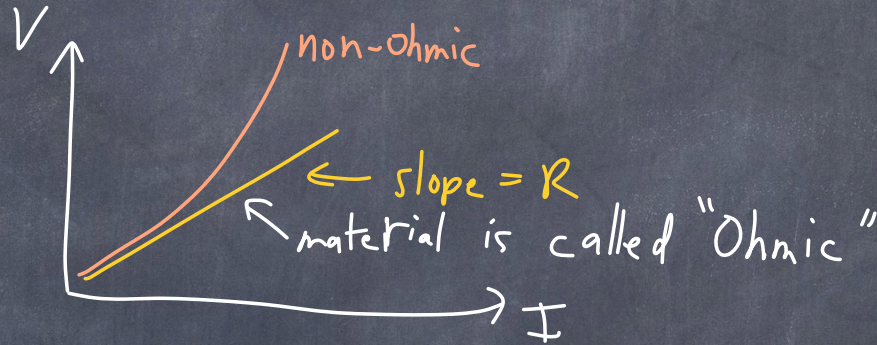


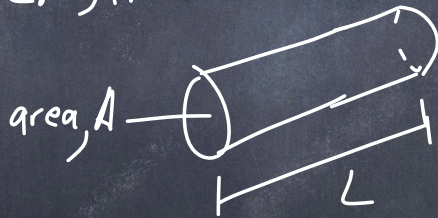The resistance R depends on the material, area, length



$$R = \frac{L}{A} \rho$$

per material
"rho" is the resistivity

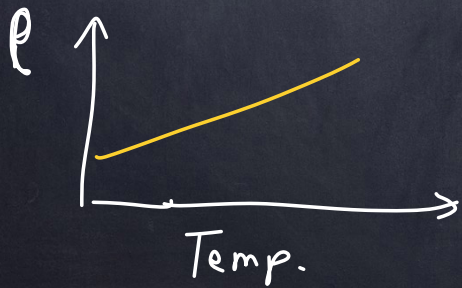

$$\rho = \rho_{20} \left[1 + \alpha (t_c - 20^\circ) \right]$$

resistivity
at 20°C
Temp. in Celsius

<u>material</u>	<u>$\rho_{20} [\Omega \cdot m]$</u>	<u>$\propto \left[\frac{1}{\rho} \right]$</u>
copper	$1.7 E-8$	$3.9 E-3$
aluminum	$2.8 E-8$	$3.9 E-3$
wood	$10^8 - 10^{14}$	
glass	$10^{10} - 10^{14}$	


If R is small, then $I = \frac{V}{R}$ is big
 more current in a copper tube
 than in a wooden one.

$$V = 4.5 V$$


$$I = 0.4 mA = 0.0004 A$$

sometimes people use
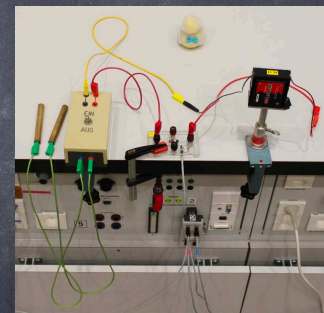
$$\text{Conductivity} = \frac{1}{\text{resistivity}}$$



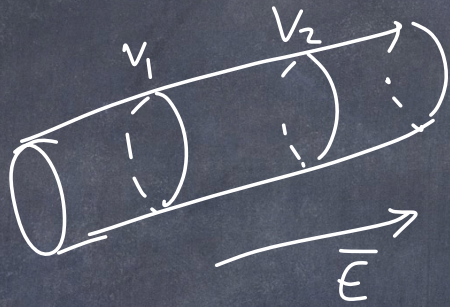Energy is lost in a conductor as electrical energy is converted into thermal energy.



Potential decrease from V_1 to V_2
 $V = V_1 - V_2$

Loss in energy $\Delta U = \Delta Q (V_2 - V_1)$

ΔQ is the amount of charge flowing from V_1 to V_2

In time Δt , $\frac{\Delta U}{\Delta t} = \frac{\Delta Q(V)}{\Delta t}$

↑
power
[Watts]

↑
[Amps]

↑
[volts]

V is the potential difference here

1 Watt = 1 Amp · Volt = 1 A·V

$$P = IV$$


power

Since we know $V = IR$ ↑

$$P = I^2 R = \frac{V^2}{R}$$

The energy loss depends on R .
 At constant I , a higher R produces more heat generated.
 At constant V , a higher R produces less heat.

Resistors in series:

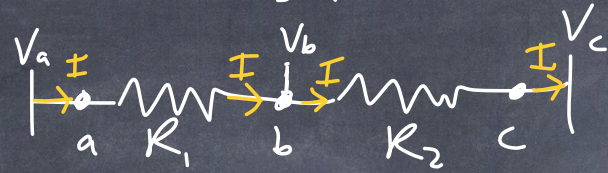

Equivalent resistance $R_{eq} = R_1 + R_2 + \dots$


$$V_b = V_a - IR_1$$

$$V_c = V_a - IR_1 - IR_2$$

$$I_a = I_b = I_c = I$$

potential decreases,
but
the current
stays the same.

Resistors in parallel:

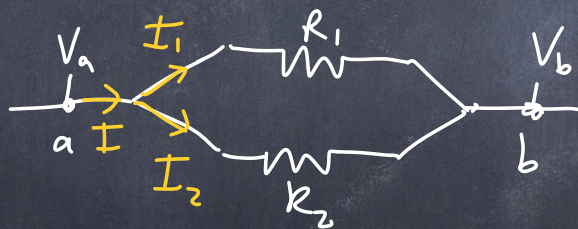


$$I = I_1 + I_2$$

Equivalent resistance
decreases (more ways for
the current to flow)

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

voltage drop $V_a - V_b$ is the
same across both pathways


$$V_{ab} = V_a - V_b = I_1 R_1 = I_2 R_2$$

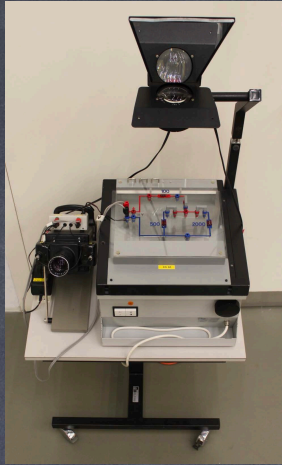


ES62




ES28

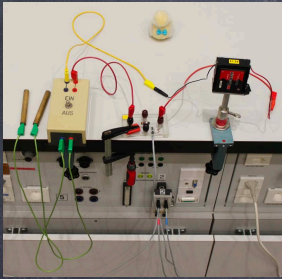


ES70

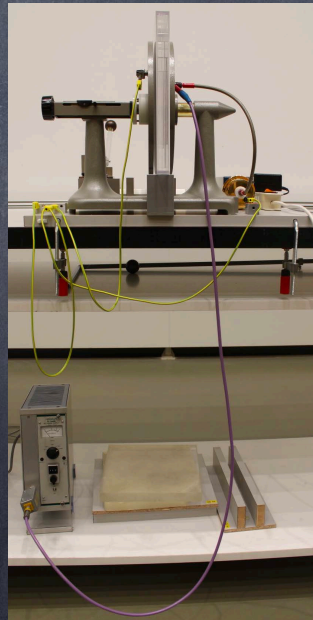

ES44

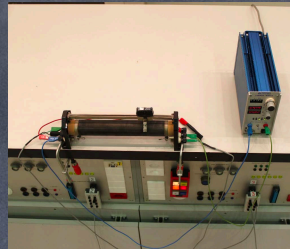

ES61

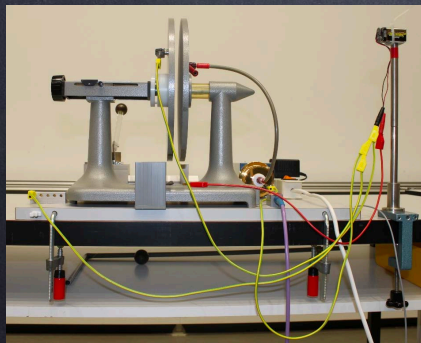

ES34